

UNCLASSIFIED

AD 402 062

DEFENSE DOCUMENTATION CENTER

FOR

SCIENTIFIC AND TECHNICAL INFORMATION

CAMERON STATION, ALEXANDRIA, VIRGINIA



UNCLASSIFIED

NOTICE: When government or other drawings, specifications or other data are used for any purpose other than in connection with a definitely related government procurement operation, the U. S. Government thereby incurs no responsibility, nor any obligation whatsoever; and the fact that the Government may have formulated, furnished, or in any way supplied the said drawings, specifications, or other data is not to be regarded by implication or otherwise as in any manner licensing the holder or any other person or corporation, or conveying any rights or permission to manufacture, use or sell any patented invention that may in any way be related thereto.

402062

17511

44345

S/142/62/005/006/008/011
E192/E382

ASTIA FILE COPY

93250
STEP

AUTHOR: Tetel'baum, Ya.I.

TITLE: Voltage ripple in full-wave rectifiers with a capacitative filter

PERIODICAL: Izvestiya vysshikh uchebnykh zavedeniy, Radiotekhnika, v. 5, no. 6, 1962, 723 - 733

TEXT: Accurate formulae and graphs for calculating the percentage ripple in full-wave rectifier circuits with a capacitative output filter are given. First, three bridge-type rectifier circuits (see Fig. 1) are considered. The percentage ripple for the k-th harmonic in these can be calculated from the formula:

$$k_{nk} = k_{\pi ko} \zeta \left(km_{\pi}, k \frac{r_a}{r_H} \right) \quad (1)$$

where $k_{\pi ko} = 20/\pi km_{\pi} C_0 r_H^{\alpha}$ is the ripple factor for an ideal rectifier in which the internal resistance r_a is much smaller than the load r_H ; ζ is a correction factor taking into account

Card 1/4

S/142/62/005/006/008/011
E192/E382

Voltage ripple

the losses due to a finite r_a and m_{π} is the ratio of the basic frequency of the rectified voltage to that of the input (at the secondary of the rectifier transformer). Curves giving ζ as a function of kr_a/r_H are illustrated in Fig. 2 and these can be used for practical calculations. Graphs can also be employed for single-phase and three-phase voltage-doubler circuits. The graphs and Eq. (1) were verified experimentally by constructing a three-phase bridge rectifier circuit and a three-phase doubler system. The measured results were in good agreement with the calculated curves. For approximate calculations it is possible to use the formula:

$$k_{\pi 1} = N/C_0 r_H \quad (12)$$

where C_0 is the capacitance of the filter in μF and r_H is the load in $k\Omega$; N is a coefficient which is dependent on the rectifier system and on the ratio r_a/r_H . For a full-wave rectifier $N = 2.9 - 2.5$ and for single-phase doubler circuits

Card 2/4

S/142/62/005/006/008/011
E192/E382

Voltage ripple

it is 2.8 - 2.2. $N = 0.48 - 0.32$ for three-phase circuits, while for three-phase doublers $N = 0.15 - 0.07$. It is pointed out that, other conditions being equal, the use of doubler circuits results in a reduction of the ripple. Thus, if in the doubler circuit the ripple is 0.5% for currents of up to 280 mA, this increases two- or threefold in a bridge circuit for output currents ranging from 100 - 280 mA. There are 6 figures and 1 table.

ASSOCIATION: Kafedra promyshlennoy elektroniki Kiyevskogo ordena Lenina politekhnicheskogo instituta (Department of Industrial Electronics of the Kiyev Order of Lenin Polytechnical Institute)

SUBMITTED: November 15, 1961

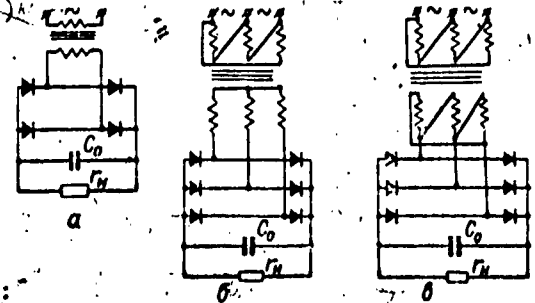



Fig. 1:

Card 3/4

S/142/62/005/006/008/011
E192/E382

Voltage ripple

Fig. 2:

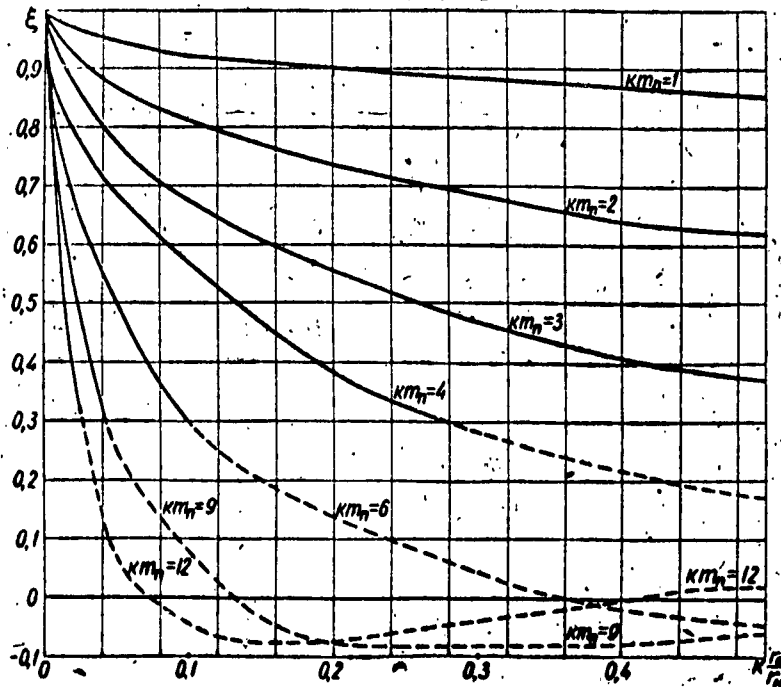

Card 4/4

Figs 1 and 2 (11.723.724) 1961.01.15